
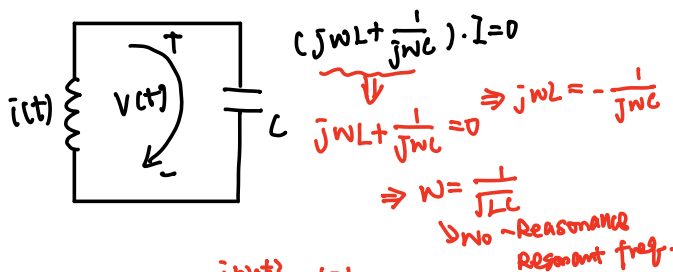




lect11 Part1 Resonance \rightarrow interpret

Mechanical Resonance \rightarrow 机械上的共振

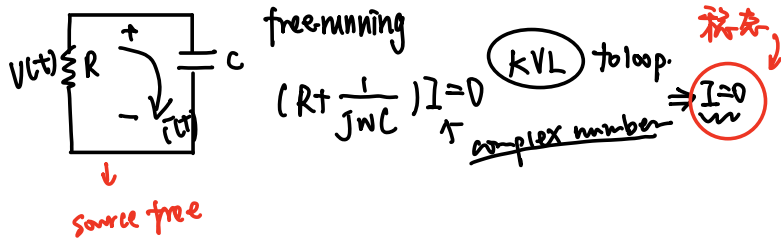

$$i(t) = \text{Re}\{I_0 e^{j\omega t}\} = |I| \cos(\omega t + \theta)$$

$$v(t) = \text{Re}\{\frac{2}{j\omega C} e^{j\omega t}\} = \frac{|I|}{\omega C} \sin(\omega t + \theta)$$

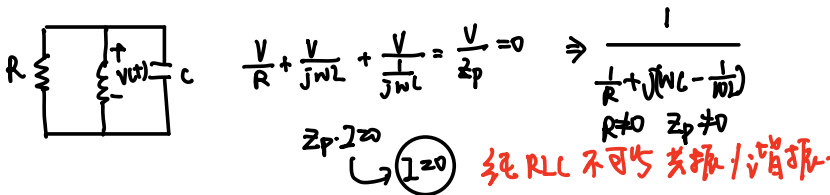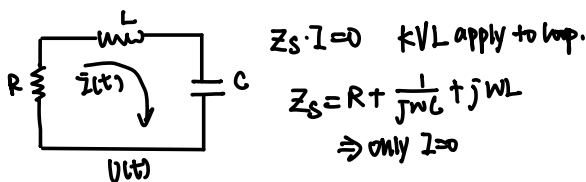

$$\omega = \frac{1}{\sqrt{LC}} \text{ can cancel the tune.}$$

Freq. domain response of LTI system.

dissipate LTI system with a \cos steady source


$$f(t) = \text{Re}\{F e^{j\omega t}\} = |F| \cos(\omega t + \angle F)$$

$$f(t) \rightarrow \boxed{\text{LTI}} \rightarrow y(t)$$

$$y(t) = \text{Re}\{Y e^{j\omega t}\} = |Y| \cos(\omega t + \angle Y)$$

$$Y = H(\omega) F \quad Y \text{ is proportional to } F \text{ through } H(\omega)$$

\hookrightarrow freq response of ckt.

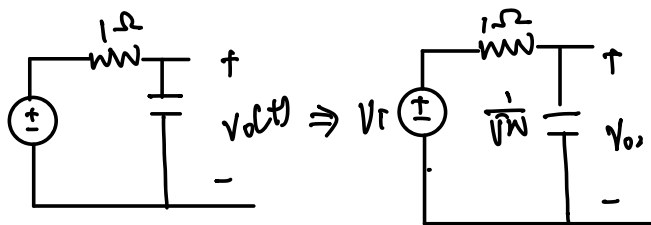


freq response.

$$F = \frac{V_o}{V_i} = H(\omega)$$

$$V_o = \frac{1/j\omega}{1 + 1/j\omega} V_i \rightarrow \frac{V_o}{V_i} = \frac{1}{1 + j\omega}$$


$$|H(\omega)| = \frac{1}{\sqrt{1 + \omega^2}}$$
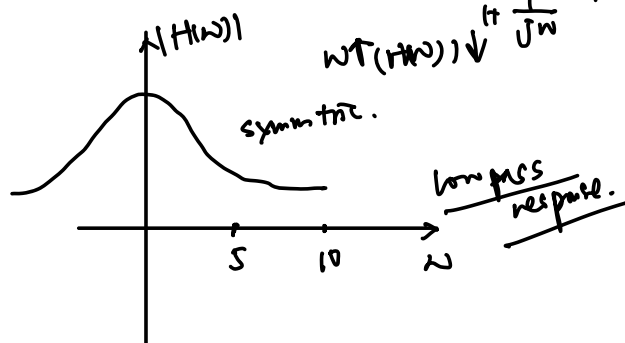
$$\angle H(\omega) = \tan^{-1}\left(\frac{-j\omega}{1 + j\omega^2}\right)$$



symmetric.

low pass response.

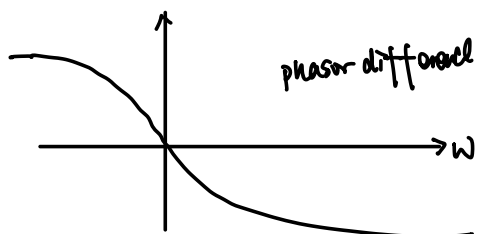


phase difference

Comments



1. An input signal with freq. near zero pass with nearly unity scaling at the output.
2. Input at higher freqs. will be attenuated.
3. low-pass filter of lowest order.
3. The phase of $H(\omega)$ depends on frequency. phase of output is retarded by 90° at high enough freq.

Example

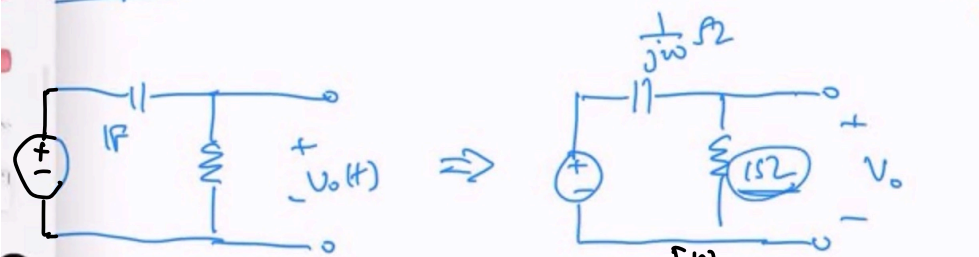

$$V_o = \frac{1}{1 + 1/j\omega} V_i \Rightarrow \frac{V_o}{V_i} = H(\omega) = \frac{j\omega}{1 + j\omega}$$



$$|H(\omega)| = \frac{|\omega|}{\sqrt{1 + \omega^2}} \quad \angle H(\omega) = \tan^{-1} \frac{1}{\omega}$$

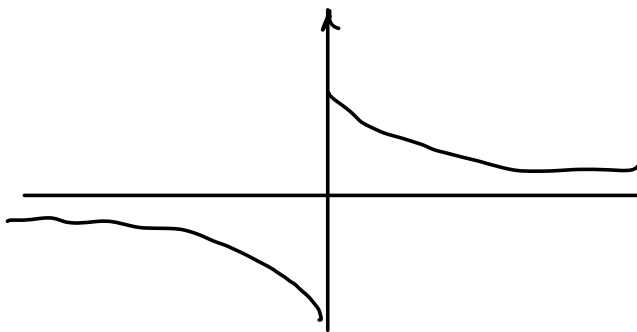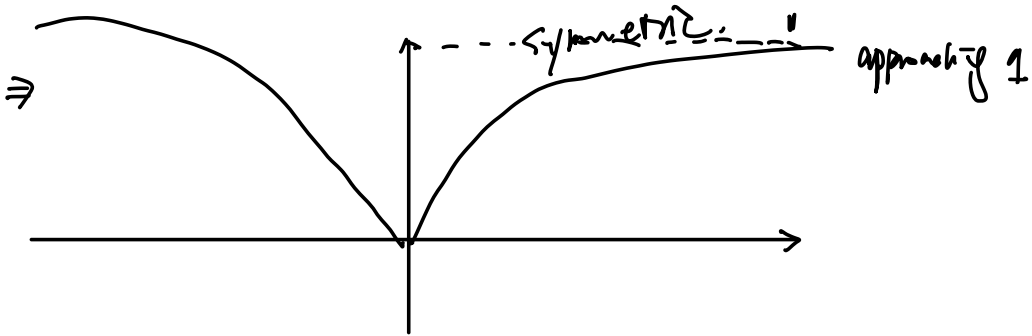

① high pass filter of lowest order.

② phase of output advances by 90° .

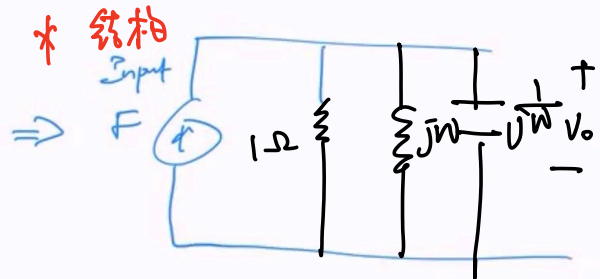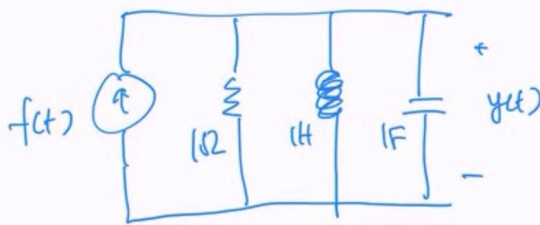③ at very high freq output almost the same as input.



$$Y = Z_{pF}$$

$$F = \frac{1}{1 + \frac{1}{j\omega} + j\omega} = \frac{j\omega}{j\omega + 1 - \omega^2} \quad H(\omega) = \frac{Y}{F} = \frac{j\omega}{1 - \omega^2 + j\omega} \Omega$$

$$|H(\omega)| = \frac{|j\omega|}{|1 - \omega^2 + j\omega|} = \frac{\omega}{\sqrt{(1 - \omega^2)^2 + \omega^2}}$$

$$\angle H(\omega) = \tan^{-1} \frac{1 - \omega^2}{\omega}$$

band pass filter.

⇒

