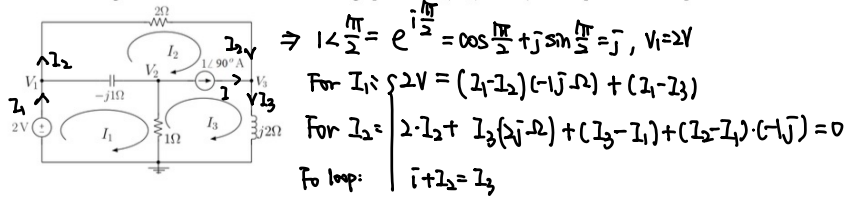


1. In the following circuit determine the node-voltage phasors V_1 , V_2 , and V_3 and express them in polar form.



$$\Rightarrow \begin{cases} 2V = -jI_1 + jI_2 + I_3 - I_2 \\ 2I_2 + 2jI_3 + I_3 - I_1 - jI_2 + jI_1 = 0 \\ I_3 I_2 = j \end{cases}$$

$$\begin{cases} (j-1)I_1 + (2-j)I_2 + (1+2j)I_3 = 0 \\ (1-j)I_1 + jI_2 - I_3 = 2 \\ 0I_1 - I_2 + I_3 = j \end{cases}$$

$$\Rightarrow 1 \angle \frac{\pi}{2} = e^{j\frac{\pi}{2}} = \cos \frac{\pi}{2} + j \sin \frac{\pi}{2} = j, V_1 = 2V$$

$$\text{For } I_1: 2V = (I_1 - I_2)(-1j\Omega) + (I_1 - I_3)$$

$$\text{For } I_2: 2I_2 + I_3(2j\Omega) + (I_3 - I_1) + (I_2 - I_1)(-1j) = 0$$


$$\text{For loop: } I_1 + I_2 = I_3$$

$$\Rightarrow \begin{cases} V_1 = 2V = 2 \angle 0^\circ \\ V_2 = 0.5 + 0.5j = \frac{\sqrt{2}}{2} \angle \frac{\pi}{4} \\ V_3 = 2jV = 2 \angle \frac{\pi}{2} \end{cases}$$

2. In the circuit shown for Problem 1, determine the loop-current phasors I_1 , I_2 , and I_3 and express them in polar form.

$$\Rightarrow \begin{bmatrix} j-1 & 2-j & 1+2j \\ 1-j & j & -1 \\ 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 2 \\ j \end{bmatrix} \Rightarrow \begin{cases} I_1 = \frac{3+j}{2} A = \frac{3}{2} + \frac{j}{2} = \frac{\sqrt{10}}{2} \angle \arctan \frac{1}{3} \\ I_2 = (1-j)A = \sqrt{2} \angle -\frac{\pi}{4} \\ I_3 = 1 \quad A = \angle 0 \end{cases}$$

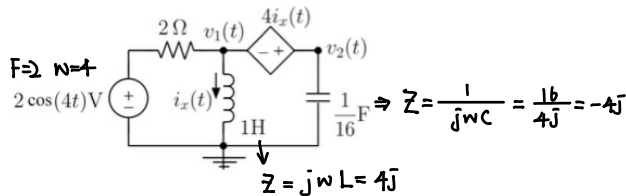
3. Use the phasor method to determine $v_1(t)$ in the following circuit:



$$\Rightarrow \begin{cases} \frac{2-V_1}{2} = \frac{V_2}{-4j} + \frac{V_1}{4j} \\ \frac{V_1}{4j} \cdot 4 = (V_2 - V_1) \end{cases} \Rightarrow \begin{cases} 2j(2-V_1) = -V_2 + V_1 \\ -jV_1 = V_2 - V_1 \end{cases}$$

$$\Rightarrow \begin{cases} (1+2j)V_1 - V_2 = 4j \\ (j-1)V_1 + V_2 = 0 \end{cases} \Rightarrow \begin{cases} V_1 = \frac{4}{3} \\ V_2 = \frac{4}{3} - \frac{4}{3}j \end{cases} \Rightarrow \begin{cases} V_1(t) = \frac{4}{3} \operatorname{Re}\{e^{j\omega t}\} \\ = \frac{4}{3} \cos 4t \end{cases}$$

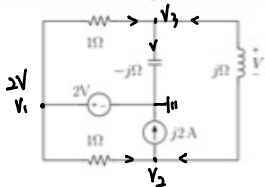4. In the following circuit determine the phasor V and express it in polar form:



$$\begin{cases} \frac{2-V_3}{1} + \frac{V_2-V_3}{j} = \frac{V_3}{-j} \\ 2j = \frac{2-V_2}{1} + \frac{V_3-V_2}{j} \end{cases}$$


$$\begin{cases} \frac{2-V_2}{1} + \frac{2-V_3}{1} = 2j + jV_3 \\ j(0V_2 - V_2) + 1-V_3 = jV_3 \end{cases}$$

$$= V_2 = \frac{8-j}{5} \Rightarrow V = \frac{-4-2j}{5}$$




$$V_3 = \frac{4-8j}{5}$$

$$= -\frac{2}{5}(2+j) = -\frac{2\sqrt{5}}{5} \angle \arctan \frac{1}{2}$$

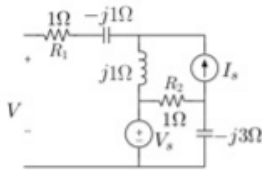5. Use the following network to answer (a) through (d):



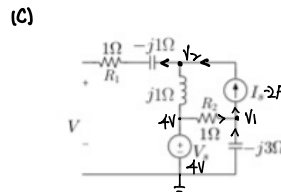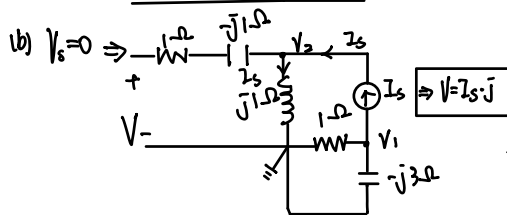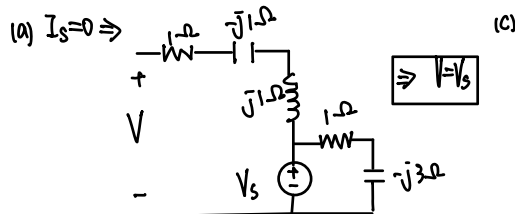- Determine the phasor V when $I_s = 0$.
- Determine the phasor V when $V_s = 0$.
- Determine V when $V_s = 4\text{ V}$ and $I_s = -2\text{ A}$, and calculate the average power absorbed in the resistors.
- What is the Thevenin equivalent and the available average power of the network when $V_s = 4\text{ V}$ and $I_s = -2\text{ A}$?



$$\begin{aligned} \Rightarrow \begin{cases} \frac{-V_1}{-3j} + \frac{4-V_1}{1} = -2A \\ \frac{V_1-4}{j1-\Omega} = -2A \end{cases} \\ \Rightarrow \begin{cases} V_1 = \frac{54-18j}{10} \text{ V} \\ V_2 = 4-2j \text{ V} \end{cases} \end{aligned}$$

$$\begin{aligned} \Rightarrow I &= \frac{V_1 - 4}{R} = \frac{14-18j}{10} \text{ A} \\ \Rightarrow P_{avg} &= \frac{1}{2} \operatorname{Re} \left\{ \frac{14-18j}{10} \cdot \frac{14+18j}{10} \right\} \\ &= \frac{1}{2} \times \frac{26}{5} = \frac{13}{5} \text{ W} \end{aligned}$$

(d) short the ckt,

$$\begin{aligned} \Rightarrow \begin{cases} \frac{-V_1}{-3j} + \frac{4-V_1}{1} = -2A \\ \frac{V_1-0}{1-j} = \frac{4-V_1}{j} \end{cases} \end{aligned}$$

$$\Rightarrow \begin{cases} V_1 = \frac{54-18j}{10} \\ V_2 = 2-6j \end{cases}$$

$$\Rightarrow I = \frac{2-6j}{1-j} = 4-2j \text{ V}$$

$$\Rightarrow R = \frac{4-2j}{4-2j} = 1\Omega$$

$$\Rightarrow \begin{aligned} & \text{Thevenin equivalent circuit} \\ & F = 4-2j \end{aligned}$$

$$\begin{aligned} \Rightarrow P_{ava} &= \frac{|V_1|^2}{8R} \\ &= \frac{4^2+2^2}{8} = \frac{5}{2} \text{ W} \end{aligned}$$

6. Determine the impedance Z_L of a load that is matched to the following network at terminals a and b , and determine the net power absorbed by the matched load. Obtain the available power of the circuit.

