
ZJU-UIUC Institute

ECE-210 ANALOG SIGNAL PROCESSING: MIDTERM

& ECE-211 ANALOG SIGNAL PROCESSING: FINAL EXAM

Instructor: Prof. Yang Xu & Prof. Songbin Gong

April 7th (Thursday), 2022

Time: 100 minutes (10:00AM – 11:40AM)

NAME: Hong Jia dong Student ID: 3200110920

INSTRUCTIONS

1. The first page of this paper should be filled clearly.
2. Calculator is permitted.
3. Access to internet is not permitted in addition to asking questions in the Wechat group, downloading and submitting the paper.
4. Solutions should be written clearly either on paper or on Pad.
5. Convert the finished paper to PDF version and submit it in the Blackboard. The submission deadline is 11:50am.

Question #	Full Marks	Your Score
1. KCL & KVL	15	
2. Thevenin Theorems & Max Power Transfer	15	
3. Op-amplifier	15	
4. Op-amplifier & 1 st Order RC Circuit	20	
5. Impedance/Admittance & Phasors Diagrams	20	
6. Superposition in Phasors	15	
Total	100	

Question 2:

In the following circuit in *Figure 2*, R_L is an adjustable resistor. It is observed that for $i = 2A$, $v = 6V$ and $R_L = R$, $i_L = 1A$ while for $i = 4A$, $v = 4V$ and $R_L = 2R$, $i_L = 9/8A$.

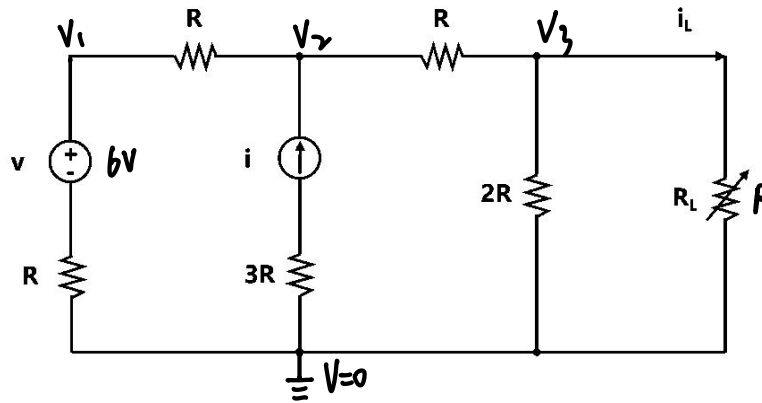


Figure 2

$$\begin{aligned}
 (a) \Rightarrow \frac{V_1 - V_2}{R} &= \frac{V_2 - V_3}{R} \\
 \frac{V_2 - V_1}{R} + \frac{V_2 - V_3}{R} &= i = 2A \\
 \frac{V_2 - V_3}{R} &= \frac{V_2}{2R} + \frac{V_3}{R} \\
 \frac{V_2}{R} &= 1A \\
 \Rightarrow \begin{cases} V_1 = 8V \\ V_2 = 10V \\ V_3 = 4V \\ R = 4\Omega \end{cases}
 \end{aligned}$$

(a) Determine the value of resistances R .

(b) Determine i_L when $i = 3A$, $v = 2V$ and $R_L = 2R$.

(c) Determine the value of resistances R_L in order to get maximum power in R_L when $i = 3A$ and $v = 2V$.

I_{short} :


$$(b) \Rightarrow \begin{cases} \frac{V_1 - V_2}{4} = \frac{V_2 - V_3}{4} \\ \frac{V_2 - V_1}{4} + \frac{V_2 - V_3}{4} = 3A \\ V_3 = 0 \end{cases} \Rightarrow \begin{cases} 2V_1 - V_2 = 2 \\ -V_1 + 2V_2 - V_3 = 12 \\ V_3 = 0 \end{cases}$$

$$\Rightarrow \begin{cases} V_1 = \frac{16}{3}V \\ V_2 = \frac{26}{3}V \end{cases} \Rightarrow I_{short} = \frac{V_2 - V_3}{4} = \frac{26}{12} = \frac{13}{6}A$$

V_{open} :

$$\begin{aligned}
 &\begin{cases} \frac{V_1 - V_2}{4} = \frac{V_2 - V_3}{4} \\ \frac{V_2 - V_1}{4} + \frac{V_2 - V_3}{4} = 3A \\ \frac{V_2 - V_3}{4} = \frac{V_3}{8} \end{cases} \Rightarrow \begin{cases} 2V_1 - V_2 = 2 \\ -V_1 + 2V_2 - V_3 = 12 \\ 2V_2 - 3V_3 = 0 \end{cases} \Rightarrow \begin{cases} V_1 = \frac{44}{5}V \\ V_2 = \frac{28}{5}V \\ V_3 = \frac{16}{5}V \end{cases} \\
 &\Rightarrow V_{open} = 10.4V \\
 &\Rightarrow \text{If } R_L = 2R = 8\Omega \\
 &\quad \therefore I_L = \frac{10.4}{8 + 8} = \frac{13}{16}A
 \end{aligned}$$

$$(c) R_L = 4.8\Omega$$

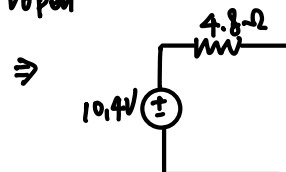


Question 3:

Design an op-amp circuit that performs the following operation

$$v_0 = 2v_1 - 3v_2$$

Notice:

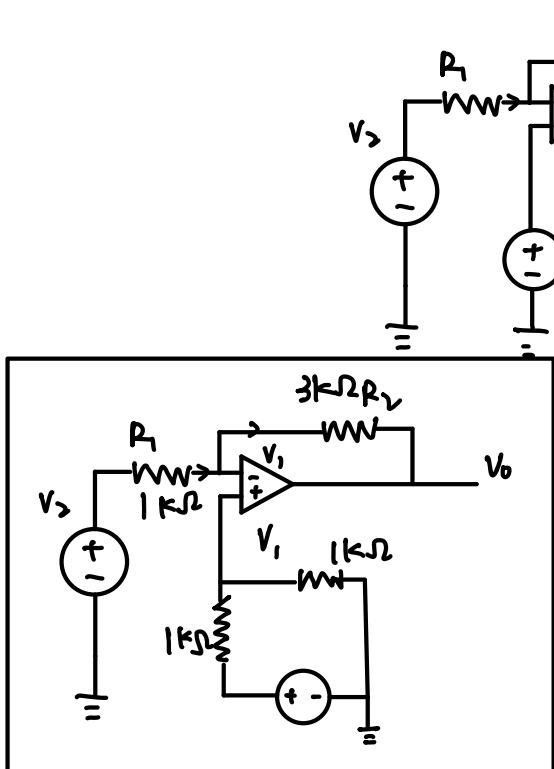1. Only one operational amplifier that you can use in this circuit.
2. All resistances must $\geq 1k\Omega$ and $\leq 100k\Omega$.



$$\Rightarrow \frac{V_1 - V_0}{R_2} = \frac{V_2 - V_1}{R_1}$$

$$\Rightarrow V_0 = V_1 - \frac{R_2}{R_1}(V_2 - V_1)$$

$$= V_1 - \frac{R_2}{R_1}V_2 + \frac{R_2}{R_1}V_1$$

$$= \left(1 + \frac{R_2}{R_1}\right)V_1 - \frac{R_2}{R_1}V_2$$

$$\Rightarrow 1 + \frac{R_2}{R_1} = 2 \quad \frac{R_2}{R_1} = 1$$

cannot operate such operation

$$\Rightarrow k \left(1 + \frac{R_2}{R_1}\right) = 2$$

$$\leftarrow \frac{R_2}{R_1} = 3 \quad \Rightarrow k = \frac{1}{2}$$

Question 4:

Write the 1st order ODE in the RC circuit, and determine $v_o(t)$ for $t > 0$ in Figure 4.

Let $v_{in} = 3u(t)$ V, and assume that capacitor is initially uncharged. ($u(t)$ is unit step function)

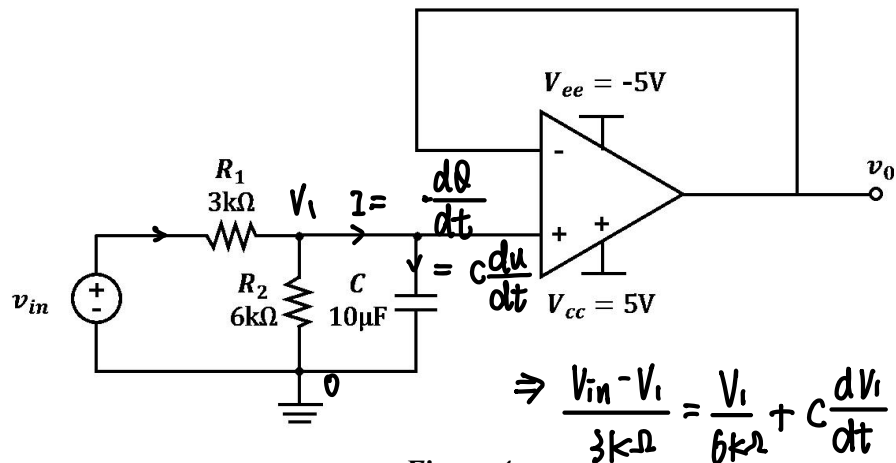


Figure 4

$$(ODE) \quad 10 \times 10^{-6} \frac{dv_1}{dt} + \frac{v_1}{6 \times 10^3} = \frac{v_{in}}{3 \times 10^3}$$

$$\Rightarrow \frac{dv_1}{dt} + 50v_1 = \frac{100}{3}v_{in}$$

$$\Rightarrow \frac{dv_1}{dt} + 50v_1 = 100u(t)$$

$$v_1 = \left(\int f(t) e^{\int 50 dt + C} \right) e^{-\int 50 dt}$$

$$= \left(\int 100 u(t) e^{50t} dt + C \right) e^{-50t}$$

$$v_1 = v_o(t) \Rightarrow v_o(t) = \left(\int_0^t 100 u(t) e^{50t} dt \right) \cdot e^{-50t}$$

Question 5:

5.1 In *Figure 5(a)*, determine the equivalent impedance of the network if the frequency $f=60$ Hz. Then, compute the current $i(t)$ if the voltage source is $v(t) = 50\cos(\omega t + 30^\circ)$.

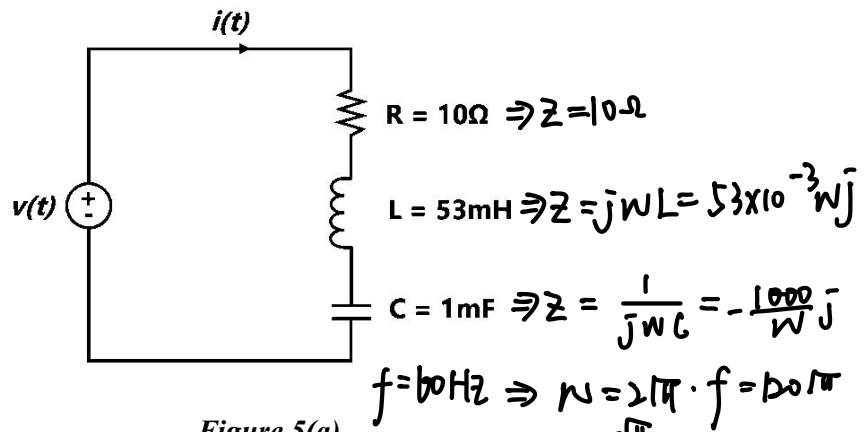


Figure 5(a)

$$\begin{aligned}
 \Rightarrow Z_L &= \frac{159}{25} \pi \cdot e^{j\frac{\pi}{2}} \\
 Z_C &= 216526 e^{-j\frac{\pi}{2}} \\
 V(t) &= 50 e^{j(120\pi t + \frac{\pi}{6})} \\
 \Rightarrow V &= 50 e^{j\frac{\pi}{6}} \\
 \Rightarrow \bar{I} &= \frac{V}{Z_R + Z_L + Z_C} \approx 25 e^{-j0.5238 \text{ rad}} \\
 \Rightarrow \bar{i}(t) &= 25 e^{-j0.5238} \cdot e^{j120\pi t} \\
 &= 25 \cos(120\pi t - 0.5238)
 \end{aligned}$$

5.2 In Figure 5(b), $i(t) = 10\cos(500t)$. Find the value of C such that $v(t)$ and $i(t)$ are in phase. Then sketch the phasor diagram for the network shown in Figure 5(b). (Hint: Here 'in phase' refers to $\theta_v = \theta_i$)


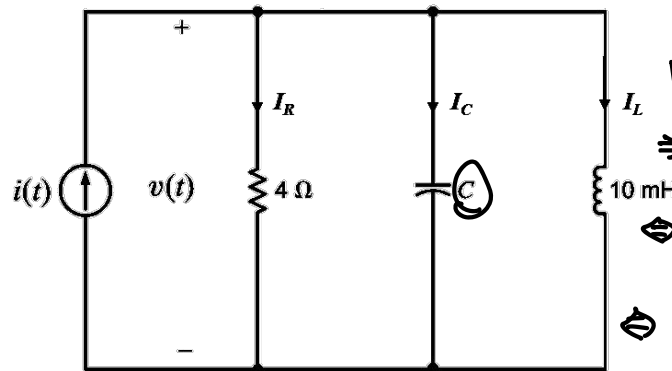


Figure 5(b)

V_t & I_t in phase

\Rightarrow Resonance.
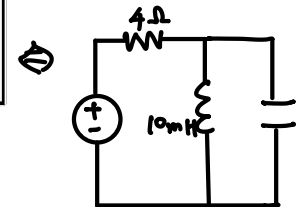
$$\Rightarrow I_C + I_L = \text{Re}\{I_C + I_L\}$$



$$\Rightarrow Z_H = j\omega L = 500 \cdot 10^{-2} \cdot j = 5j$$

$$Z_C = -5j$$


$$\Rightarrow \frac{1}{j\omega C} = -5j$$

$$\therefore \frac{1}{500 \cdot C} = +5j$$


$$\therefore C = \frac{1}{2500}$$

Question 6:In *Figure 6*,

- 1) Use superposition to find V_o in the network in *Figure 6*.
- 2) Express time-domain output voltage $V_o(t)$.

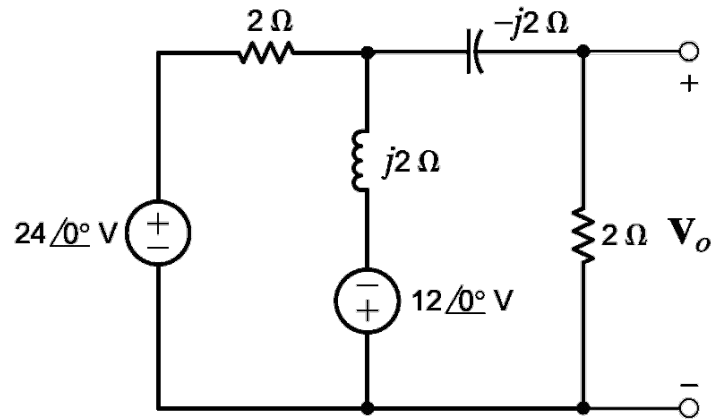*Figure 6*

ii)

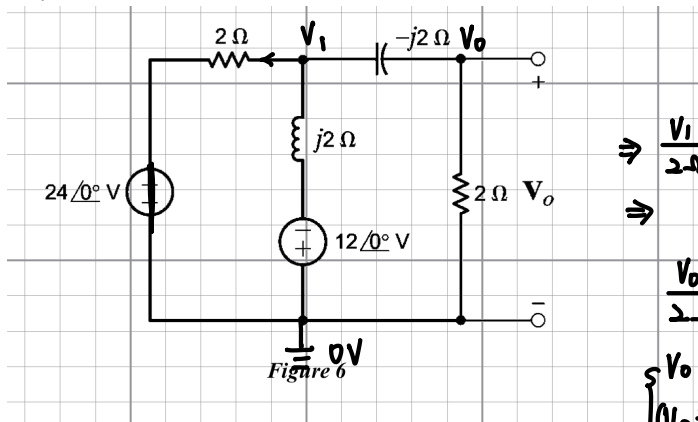


$$\Rightarrow \frac{V_1}{2\Omega} + \frac{V_1 - V_o}{-j2\Omega} = \frac{-12 - V_1}{j2\Omega}$$

$$\Rightarrow (V_o + 12)j = V_1$$

$$\frac{V_o}{2\Omega} = \frac{V_1 - V_o}{-j2\Omega}$$
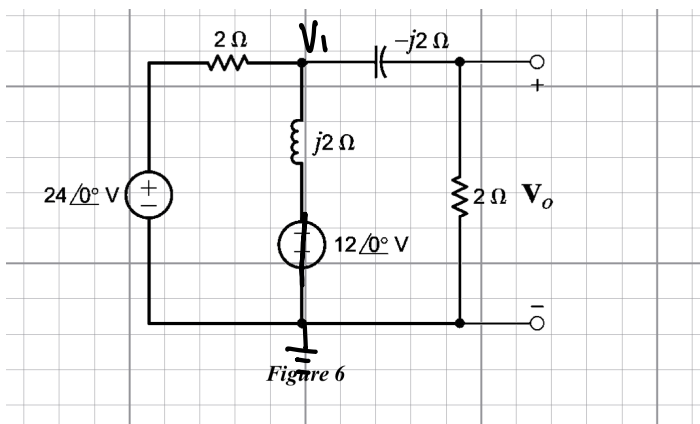
$$\begin{cases} V_o = (V_1 - V_o)j \\ (V_o + 12)j = V_1 \end{cases} \Rightarrow V_o = -\frac{24}{5} + \frac{12}{5}j$$



$$\frac{V_1}{j2} + \frac{V_1 - V_o}{-j2} = \frac{24}{2}$$

$$\Rightarrow \frac{V_o}{2j} = 12$$

$$\Rightarrow V_o = 24j$$

$$\begin{aligned} \Rightarrow V_o &= \frac{-24}{5} + 24j \\ &= 12\sqrt{5} e^{j1.175} \end{aligned}$$

$$\Rightarrow V(t) = 12\sqrt{5} \cos(\omega t + 1.175 \text{ rad})$$

Formula Sheet

Table 1. Suggestions for particular solutions of $\frac{dy}{dt} + ay(t) = bf(t)$ with various source functions $f(t)$.

	Source function $f(t)$	Particular solution of $\frac{dy}{dt} + ay(t) = bf(t)$
1	constant D	constant K
2	Dt	$Kt + L$ for some K and L
3	De^{pt}	Ke^{pt} if $p \neq -a$ Kte^{pt} if $p = -a$
4	$\cos(\omega t)$ or $\sin(\omega t)$	$H \cos(\omega t + \theta)$, where H and θ depend on ω , a , and b