

lect. 9

$$5 \cos(5t + \frac{\pi}{3})$$

A

$$\Rightarrow 5 \angle \frac{\pi}{3} \Rightarrow \text{phasor}$$

$$F \Rightarrow f(t) \text{ Re}\{F \cdot e^{j\omega t}\}$$

time invariant & Linear LTI system.

$$\text{Re}\{5e^{j(5t + \frac{\pi}{3})}\} \Rightarrow 5 \cos(5t + \frac{\pi}{3})$$

Derivative Principle

$$f(t) = \text{Re}\{F \cdot e^{j\omega t}\} \xrightarrow{\text{phasor}} f(t) \frac{df(t)}{dt} = ?$$

$$\frac{df(t)}{dt} = \frac{d \text{Re}\{F \cdot e^{j\omega t}\}}{dt} = \text{Re}\left\{\frac{d}{dt} F e^{j\omega t}\right\}$$

complex number const.

$$= \text{Re}\left\{F \frac{d e^{j\omega t}}{dt}\right\} = \text{Re}\{F j\omega e^{j\omega t}\} = \text{Re}\{j\omega F e^{j\omega t}\}$$

$$\left. \begin{aligned} f(t) &= \text{Re}\{F e^{j\omega t}\} \\ \frac{df(t)}{dt} &= \text{Re}\{j\omega F e^{j\omega t}\} \end{aligned} \right\} \Rightarrow \frac{df(t)}{dt} \propto j\omega F$$

other phasors.

Example.

Particular sol. of

$$\frac{dy}{dt} + 2y = 5 \sin(6t)$$

identity $\Rightarrow 5 \angle -90^\circ$

$$y(t) \rightarrow Y \quad j\omega = 6j$$

$$(j6)Y + 2Y = 5 \angle -90^\circ \Rightarrow \text{algebraic eq.}$$

$$\Rightarrow -36Y + 18jY = -5j \Rightarrow Y = \frac{-5j}{-34 + j18}$$

(分母有理化)

$$\Rightarrow (-34 + j18)Y = -5j \Rightarrow Y = \frac{-5j(-34 - j18)}{(-34 + j18)(-34 - j18)} = 0.13 \angle 117.9^\circ$$

$$y_p(t) = 0.13 \cos(6t + 117.9^\circ)$$

simplify solc. ODE for higher order

$$\text{phasor}$$

$$\begin{aligned} i(t) &= \text{Re}\{I e^{j\omega t}\} \\ v(t) &= \text{Re}\{V e^{j\omega t}\} \end{aligned} \quad \begin{aligned} v(t) &= i(t) \cdot R \\ \text{Re}\{V e^{j\omega t}\} &= \text{Re}\{I e^{j\omega t}\} \cdot R \end{aligned}$$

$\Rightarrow V = I R$ for a resistor

$\Rightarrow V = IR$ stands for phasor

$$+ \quad L \quad -$$

$$\begin{aligned} i(t) &= \text{Re}\{I e^{j\omega t}\} \\ v(t) &= \text{Re}\{V e^{j\omega t}\} \end{aligned}$$

$$V(t) = L \frac{di(t)}{dt} \Rightarrow V = j\omega L I$$

impedance \Rightarrow complex number $\frac{V}{I}$

$$+ \quad -$$

$$\begin{aligned} i(t) &= \text{Re}\{I e^{j\omega t}\} \\ v(t) &= \text{Re}\{V e^{j\omega t}\} \end{aligned} \quad \begin{aligned} i(t) &= C \frac{dv(t)}{dt} \\ I &= C \cdot j\omega \cdot V \end{aligned} \Rightarrow V = \frac{I}{j\omega C}$$

$$\begin{aligned} L &= V = j\omega L I \\ C &= \frac{1}{j\omega C} I \\ V &= R I \end{aligned}$$

$$i(t)$$

$$I \downarrow \downarrow$$

$$V = R I \quad V = \frac{1}{j\omega C} I$$

$$\text{total } V = V_R + V_C = R I + \frac{1}{j\omega C} I$$

$$\frac{V}{I} = \text{complex} = (R + \frac{1}{j\omega C})$$

Resistance \rightarrow reactance

$$\frac{I}{V} = Y \Rightarrow \text{admittance} = R + jX$$

conductance \Rightarrow susceptance

$$Z = \begin{cases} j\omega L & \text{for inductor} \\ \frac{1}{j\omega C} & \text{for capacitor} \\ R & \text{for resistor} \end{cases}$$

通低阻高 通高阻低

Impedance \rightarrow slow sth down.

admittance \Rightarrow 快

① ω -signal freq.

② Z -impedance measures in units of $\frac{V}{I}$

$\frac{V}{I}$ V to I ratio

unlike resistance/reactance $\Rightarrow Z$ a complex number

-img part of Z called reactance, $\frac{\text{imag}}{\text{real}}$ ad

-real part of Z called resistance. only resistors reactance

③ using the generalized $V-I$ relationship Z all kcl kvl in phasor form we can express LTI ckt & C with

in an algebraic form of a sinusoidal signal.

lect 9 part 2

Lect 9. Part 2.

impedance combination.

$$Z_s = Z_1 + Z_2$$

$$Z_p = \frac{Z_1 \cdot Z_2}{Z_1 + Z_2}$$



$$Z_1 = 6\Omega \quad Z_2 = j8\Omega$$

$$Z_s = 6 + j8\Omega$$

$$Z_p = \frac{6 \cdot j8}{6 + j8} = \frac{48j(-j8)}{(6-j8)(6+j8)} = \frac{384}{100} = 3.84\Omega$$

$$V = ZI$$

$$V = |V|e^{j\theta_V}$$

$$Z = |Z|e^{j\theta_Z}$$


$$|V| = |Z||I|$$

$$\theta_V = \theta_I + \theta_Z$$

→ 非线性元件, 阻抗

Phase shift → complex


voltage & current division

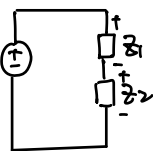

$$V_1 = \frac{Z_1}{Z_1 + Z_2} V$$


$$V_2 = \frac{Z_2}{Z_1 + Z_2} V$$

← resistive

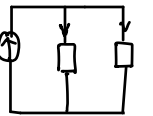

$$I_1 = I \frac{Z_2}{Z_1 + Z_2}$$

$$I_2 = I \frac{Z_1}{Z_1 + Z_2}$$

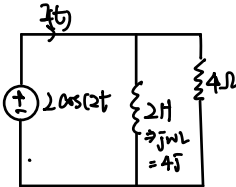


$$I = \frac{2}{4j + j4} = \frac{2}{8j} = \frac{1+j}{2}$$

$$= \frac{(1+j)-j}{2j(1-j)} = \frac{1-j}{2}$$

$$= \frac{1}{\sqrt{2}} e^{j\frac{\pi}{4}} \cdot A$$

$$\Rightarrow I(t) = \frac{1}{\sqrt{2}} \cos(2t - \frac{\pi}{4}) \quad \left| \begin{array}{l} \text{lagging} \\ \text{power} \end{array} \right|$$

Example:

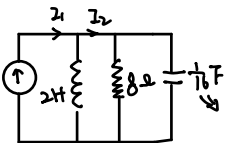

$$2 \cos(4t - \frac{\pi}{3}) \Rightarrow \omega = 4$$

$$\Rightarrow Z_p = \frac{j\omega L \cdot \frac{1}{j\omega C}}{j\omega L + \frac{1}{j\omega C}} = -8j$$


$$I_2 = \frac{8}{8-j8} \cdot I \Rightarrow \frac{1}{1-j} \cdot I$$

$$C = a + jb \quad |C| = \sqrt{a^2 + b^2} \quad |C| \angle \phi$$

$$\cos \phi = \frac{a}{|C|} \Rightarrow |C| \cdot e^{j\phi_1} \cdot |a| \cdot e^{j\phi_2}$$

$$\Rightarrow |C| \cdot |a| \cdot e^{j(\phi_1 + \phi_2)}$$

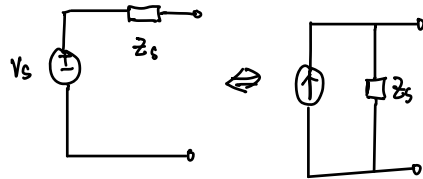Source transformation / source suppression.



$$I_s = \frac{V_s}{Z_s}$$

Example

