

$$y = Ae^{-at} + y_p(t)$$

$$y(t) = y(0^-)e^{-at} + y_p(t) - y_p(0^-)e^{-at} = [y(0^-) - y_p(0^-)]e^{-at} + y_p(t)$$

$$y_{\text{transient}}^{(t)} = [y(0^-) - y_p(0^-)]e^{-at}$$

$$y_{\text{steady}}^{(t)} = y_p(t)$$

$$y_{\text{zero input}}^{(t)} = y(0^-)e^{-at}$$


Zhejiang University – University of Illinois at Urbana-Champaign Institute

$$y_{\text{zero state}}^{(t)} = y_p(t) - y_p(0^-)e^{-at}$$

ECE-210 Analog Signal Processing Spring 2022

Homework #5: Submission Deadline 23rd March (10:00 PM)

1. Consider the following circuit with $v(0^-) = 1V$ and let $f(t) = 2e^{-t/3}V$. For $t > 0$, obtain:

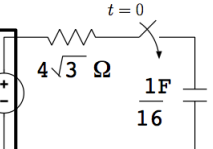c) 

As $v(0^-) = 1V$ and $f(t) = 2e^{-t/3}$

$$\Rightarrow y = \int \frac{8e^{-t/3}}{16} \cdot e^{-\frac{1}{16}t} dt + C] e^{-\frac{1}{16}t}$$

$$\Rightarrow C \frac{dv}{dt} + \frac{1}{16}v = f(t) \Rightarrow \frac{dv}{dt} + \frac{4}{15}v = \frac{4f(t)}{15} = \frac{8e^{-t/3}}{15}$$

$$y|_{t=0} = 1V$$

$$y = \frac{96+8\sqrt{3}}{47} e^{-\frac{1}{15}t} + \frac{-49-8\sqrt{3}}{47} e^{-\frac{1}{15}t}$$

(a) the zero-state voltage across the capacitor's terminals, $v_{zs}(t)$,

(b) the zero-input voltage across the capacitor's terminals, $v_{zi}(t)$,

(c) the transient voltage across the capacitor's terminals, $v_{tr}(t)$,

(d) the steady state voltage across the capacitor's terminals, $v_{ss}(t)$, and


(e) the total voltage across the capacitor's terminals, $v(t)$.

a) $v_{zs} = y_p(t) - y_p(0^-)e^{-at}$
 $= \frac{96+8\sqrt{3}}{47} e^{-\frac{1}{15}t} - \frac{96+8\sqrt{3}}{47} e^{-\frac{1}{15}t}$

b) $v_{zi} = y(0^-)e^{-at}$
 $= e^{-\frac{1}{15}t}$

2. Consider the following circuit with $f(t) = 10\cos(\omega t)$ volts and $v(0^-) = v_0$ volts.

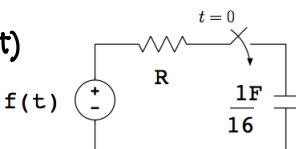(a) $\frac{R}{16} \frac{dv}{dt} + v = f(t) \Rightarrow \frac{dv}{dt} + \frac{16}{R}v = \frac{160}{R} \cos(\omega t)$



It is known that for $t > 0$, $v(t) = Ae^{-t} + B \cos(2t) + C \sin(2t)$ volts.

b) for 1st order linear ODE.

(a) Write the ODE that governs this system for $t > 0$ in terms of R , $v(t)$, and ω .

(b) Find the value of R .

(c) What is the value of ω ? \Rightarrow only term have exponential term is e^{-t}

(d) What are the values of B and C ? $\Rightarrow \int \frac{16}{R} dt = e^{-t} \Rightarrow R = 16\Omega$

(e) If $v(t)$ is the zero-state response, what is the value of A ? \Rightarrow Zero state $\Leftrightarrow y(0^-) = 0$
 $\Rightarrow V = 2\cos(2t) - 2e^{-t} + \sin(2t)$

(f) Identify $v_{tr}(t)$, the transient component of $v(t)$.

(g) Identify $v_{ss}(t)$, the steady-state component of $v(t)$.

(h) What is steady-state phasor V ? $\Rightarrow V_{ss} = 2\sqrt{5} \cos(2t - \phi), \tan \phi = 2$

3. The different parts of this problem are unrelated:

a) $N=2$ c)
 $C=4$ d)
 $B=2$
 $A=v_0=2$

(a) Show that $\frac{e^{j4t} + e^{-j4t}}{2} = \cos(4t)$.

(b) Express $\frac{e^{-j2t} - e^{j2t}}{j}$ in terms of a sine function.

(c) Express $\text{Re}\{2e^{j\frac{\pi}{3}} e^{-j5t}\}$ in terms of a cosine function.

(d) Determine the phasor F of $f(t) = -2\sin(2t - \frac{\pi}{3})$. Express F in both polar and rectangular coordinates.

(e) Determine the phasor F of $f(t) = \cos(3t - \frac{\pi}{2})$. Express F in both polar and rectangular coordinates.

(f) Express the phasor $F = 2 - j2$ in terms of a cosine function $f(t)$ having frequency $\omega = 3 \frac{\text{rad}}{\text{s}}$.

(g) Express the phasor $F = 3e^{-j\frac{\pi}{3}}$ in terms of a cosine function $f(t)$ having frequency $\omega = 3 \frac{\text{rad}}{\text{s}}$.

a) $\frac{1}{2}[e^{j4t} + e^{-j4t}]$
 $= \frac{1}{2}[\cos 4t + j\sin 4t + \cos 4t - j\sin 4t]$
 $= \cos 4t$
 Q.E.D.

b) $\frac{e^{-j2t} - e^{j2t}}{j} = \frac{1}{j}(\cos 2t - j\sin 2t - \cos 2t - j\sin 2t)$
 $= 2 \sin 2t$

(c) $\text{Re}\{2e^{j(\frac{\pi}{3}-5t)}\}$
 $= 2 \cos(\frac{\pi}{3} - 5t)$

d) $f(t) = -2\sin(2t - \frac{\pi}{3})$
 $= 2 \cos(2t - \frac{\pi}{3} + \frac{\pi}{2})$
 $= 2 \cos(2t + \frac{\pi}{6}) = \text{Re}\{2e^{j(2t + \frac{\pi}{6})}\}$
 $\Rightarrow F = 2e^{j\frac{\pi}{6}} = 2 \angle \frac{\pi}{6} = 2 \cos \frac{\pi}{6} + j2 \sin \frac{\pi}{6} = \sqrt{3} + j$

e) $f(t) = \cos(3t - \frac{\pi}{2}) = \sin 3t = \text{Re}\{e^{j(3t - \frac{\pi}{2})}\}$
 $F = e^{-j\frac{\pi}{2}} = -j$

f) $F = 2 - j2$
 $F = 2\sqrt{2} \angle -\frac{\pi}{4}$
 $f(t) = \text{Re}\{2\sqrt{2} e^{-j\frac{\pi}{4}} e^{j3t}\}$
 $= 2\sqrt{2} \cos(3t - \frac{\pi}{4})$

g) $F = 3e^{-j\frac{\pi}{3}}$
 $f(t) = \text{Re}\{3e^{-j\frac{\pi}{3}} e^{j3t}\}$
 $= 3 \cos(3t - \frac{\pi}{3})$

4. Use the phasor method to express the following signals in terms of a single cosine function:

(a) $f(t) = -3 \sin(3t) + 3 \cos(3t)$.

(b) $g(t) = 2 [\sin(2t) - \sin(2t + \pi/2)]$.

$$\begin{aligned}
 \text{(a) } f(t) &= 3 \cos(3t) - 3 \sin(3t) \\
 &= 3\sqrt{2} \left[\frac{\sqrt{2}}{2} \cos(3t) - \frac{\sqrt{2}}{2} \sin(3t) \right] \\
 &= 3\sqrt{2} \cos\left(3t + \frac{\pi}{4}\right) \\
 &= \operatorname{Re}\{3\sqrt{2} e^{j(3t + \frac{\pi}{4})}\} = \operatorname{Re}\{3\sqrt{2} e^{j\frac{\pi}{4}} e^{j3t}\} \\
 F &= 3\sqrt{2} e^{j\frac{\pi}{4}}, \omega = 3 \text{ rad/s}
 \end{aligned}$$

$$\begin{aligned}
 \text{(b) } f(t) &= 2 [\cos(2t) - \sin(2t)] \\
 &= 2\sqrt{2} \cos\left(2t + \frac{\pi}{4}\right) \\
 &= \operatorname{Re}\{2\sqrt{2} e^{j\frac{\pi}{4}} e^{j2t}\} \\
 \Rightarrow F &= 2\sqrt{2} e^{j\frac{\pi}{4}}, \omega = 2 \text{ rad/s}
 \end{aligned}$$