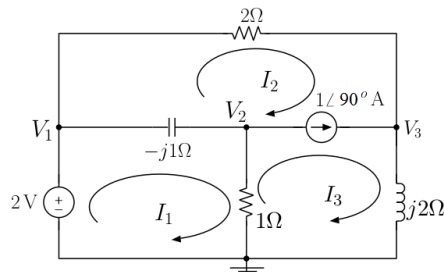


ECE-210 Analog Signal Processing Spring 2022  
Homework #6: Solution

1. In the following circuit determine the node-voltage phasors  $V_1$ ,  $V_2$ , and  $V_3$  and express them in polar form.

**Solution:**

$V_1$  can be determined directly from the circuit,

$$V_1 = 2\text{ V} = 2\angle 0^\circ \text{ V}.$$

Applying KCL at  $V_2$  gives

$$\frac{V_2}{1} + \underbrace{1\angle 90^\circ}_j + \frac{V_2 - V_1}{-j} = 0.$$

Likewise, the KCL equation at  $V_3$  is

$$\frac{V_3}{j2} + \frac{V_3 - V_1}{2} = \underbrace{1\angle 90^\circ}_j.$$

From the first KCL equation, we obtain

$$\begin{aligned} V_2 + j + j(V_2 - 2) &= 0 \\ V_2 &= \frac{j}{1+j} = \frac{e^{j\frac{\pi}{2}}}{\sqrt{2}e^{j\frac{\pi}{4}}} \\ V_2 &= \frac{\sqrt{2}}{2}e^{j\frac{\pi}{4}} \text{ V} = \frac{\sqrt{2}}{2}\angle 45^\circ \text{ V}. \end{aligned}$$

From the second KCL equation, we have

$$\begin{aligned} -jV_3 + V_3 - 2 &= j2 \\ V_3 &= \frac{2+j2}{1-j} = 2j \text{ V} = 2\angle 90^\circ \text{ V}. \end{aligned}$$

2. In the circuit shown for Problem 1, determine the loop-current phasors  $I_1$ ,  $I_2$ , and  $I_3$  and express them in polar form.

**Solution:**

From the circuit we notice that

$$V_3 = 2j \cdot I_3 = 2j$$

Therefore

$$I_3 = 1 \text{ A} = 1\angle 0^\circ \text{ A}$$

Applying KCL at  $V_3$  yields

$$I_3 - I_2 = \underbrace{1\angle 90^\circ}_j$$

Plugging in  $I_3$  we have

$$\begin{aligned} I_2 &= 1 - j = \sqrt{2}e^{-j\frac{\pi}{4}} \text{ A} \\ &= \sqrt{2}\angle -45^\circ \text{ A} \end{aligned}$$


By applying KCL at the bottom node (ground), we have

$$I_3 + \frac{V_2}{1} = I_1$$

Plugging in  $I_3$  and  $V_2$  we obtain  $I_1$

$$\begin{aligned} I_1 &= \frac{3+j}{2} \\ &= \frac{\sqrt{10}}{2} e^{j \arctan \frac{1}{3}} A \\ &= \frac{\sqrt{10}}{2} \angle 18.4^\circ A \end{aligned}$$

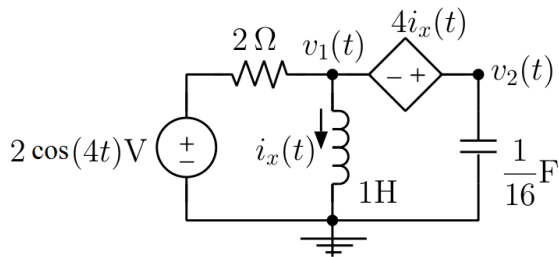3. Use the phasor method to determine  $v_1(t)$  in the following circuit:



**Solution:**

From the voltage source we know  $\omega = 4 \text{ rad/s}$ . Impedence of the capacitor is given by

$$Z_C = \frac{1}{j\omega C} = \frac{4}{j} = -4j$$

Impedence of the inductor is given by

$$Z_L = j\omega L = 4j$$

Writing the KCL equation for the super-node on top of the circuit we can obtain

$$\frac{V_1 - 2}{2} + \frac{V_1}{4j} + \frac{V_1 + 4I_x}{-4j} = 0,$$

Meanwhile from the  $V - I$  relation for the inductor's impedance we have

$$I_x = \frac{V_1}{4j},$$


Plugging in  $I_x$  to the previous equation yields

$$\begin{aligned} i_x &= \frac{1}{3j} \\ V_1 &= \frac{4}{3} \end{aligned}$$

Therefore the steady-state voltage  $v_1(t)$  can be express as

$$v_1(t) = \frac{4}{3} \cos(4t) \text{ V}.$$

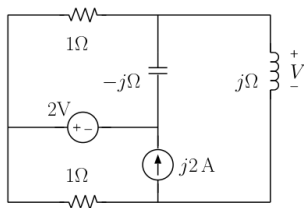4. In the following circuit determine the phasor  $V$  and express it in polar form:



**Solution:**

Denote the intersection node in the middle of this circuit by  $V_1$ . The KCL equation at the top node is given by

$$\frac{V - (V_1 + 2)}{1} + \frac{V - V_1}{-j} + \frac{V}{j} = 0,$$

which yields

$$jV + (1 - j)V_1 = 2j$$

While for the bottom node, the KCL equation is give by

$$\frac{V}{j} + \frac{V_1 + 2}{1} = 2j$$


which yields

$$jV_1 + V = -2 - 2j$$

We can obtain  $V$  by solving these two equations, which yields

$$\begin{aligned} V &= -\frac{4 + 2j}{5} \\ &= \frac{2}{\sqrt{5}} e^{j(\arctan(\frac{1}{2}) - \pi)} \text{ V} = \frac{2}{\sqrt{5}} \angle -153.4^\circ \text{ V}. \end{aligned}$$

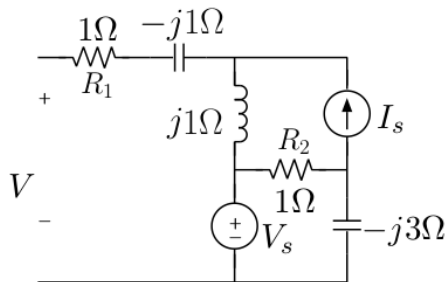5. Use the following network to answer (a) through (d):



- Determine the phasor  $V$  when  $I_s = 0$ .
- Determine the phasor  $V$  when  $V_s = 0$ .
- Determine  $V$  when  $V_s = 4 \text{ V}$  and  $I_s = -2 \text{ A}$ , and calculate the average power absorbed in the resistors.
- What is the Thevenin equivalent and the available average power of the network when  $V_s = 4 \text{ V}$  and  $I_s = -2 \text{ A}$ ?

**Solution:**

- (a) When  $I_s = 0$ , there is no current flowing through the inductor or the capacitor or the resistor  $R_1$ , therefore

$$V = V_s.$$

- (b) When  $V_s = 0$  the only current flowing through the inductor is  $I_s$ , consequently

$$V = I_s(j1) = jI_s.$$

- (c) By superposition,

$$V = V_s + jI_s = (4 - j2) \text{ V}$$

For the resistor  $R_1$ , the average absorbed power is ,

$$P_{R_1} = 0 \text{ W},$$

since no current is flowing through it. For the other resistor  $R_2$ ,

$$P_{R_2} = \frac{|V_{R_2}|^2}{2R_2}.$$

Denote the node on top of the capacitor as  $V_1$ , applying KCL at  $V_1$  gives us

$$\frac{V_s - V_1}{1} = I_s + \frac{V_1}{3j}.$$

which yields

$$V_1 = \frac{18}{3 + j}$$

Therefore the voltage across resistor  $R_2$  is given by

$$V_{R_2} = V_s - V_1 = \frac{-7 + 9j}{5} = \frac{\sqrt{130}}{5} e^{j \arctan -\frac{9}{7}}.$$


Plugging  $V_{R_2}$  into the previous equation and we can obtain  $P_{R_2}$

$$\begin{aligned} P_{R_2} &= \frac{|V_{R_2}|^2}{2R_2} = \frac{|\frac{\sqrt{130}}{5}|^2}{2} \\ &= 2.6 \text{ W}. \end{aligned}$$

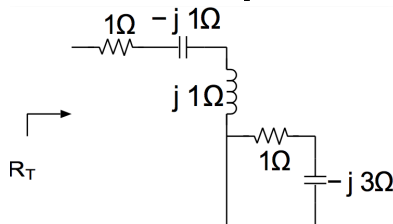(d) From part (c) we have the Thevenin Voltage

$$V_T = (4 - j2) \text{ V} = 2\sqrt{5} e^{j \arctan(-\frac{1}{2})} \text{ V}$$


For the Thevenin impedance we suppress the independent sources, yielding to the following circuit:



The Thevenin impedance is

$$Z_T = 1 \Omega.$$

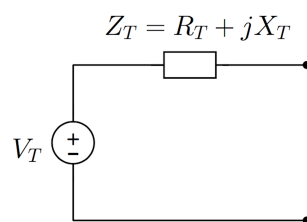
Then the Thevenin equivalent can be represented as



where  $R_T = 1$  and  $X_T = 0$ . Finally the available average power is given by

$$P_a = \frac{|V_T|^2}{8R_T} = \frac{(2\sqrt{5})^2}{8} = 2.5 \text{ W}.$$

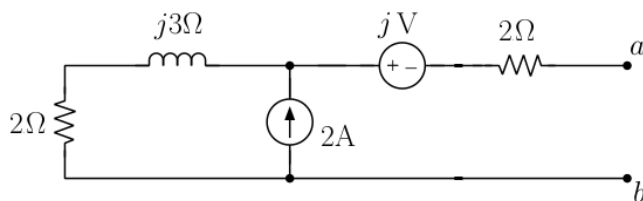6. Determine the impedance  $Z_L$  of a load that is matched to the following network at terminals  $a$  and  $b$ , and determine the net power absorbed by the matched load:



**Solution:**

To determine  $Z_L$  we first need to calculate the Thevenin impedance  $Z_T$ . Suppressing the independent sources we have

$$Z_T = j3 + 4 \Omega$$

Therefore, the matched load can be obtained as follows,

$$Z_L = Z_T^* = (4 - j3)\Omega.$$

We can obtain the Thevenin Voltage by calculating the open-circuit voltage as follows

$$V_T = 2 \cdot (j3 + 2) - j = 4 + 5j \text{ V}.$$

Thus, the net power absorbed by the matched load is the average available power,

$$P_a = \frac{|V_T|^2}{8R_T} = \frac{16 + 25}{8 \times 4} = \frac{41}{32} \text{ W}.$$