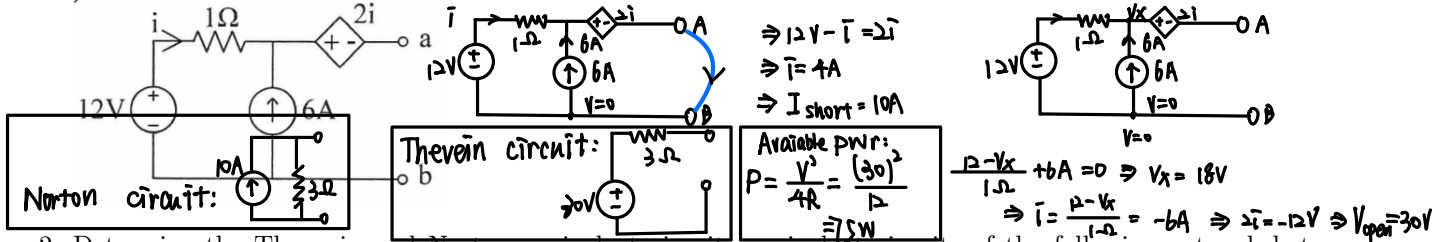



ECE-210 Analog Signal Processing Spring 2022

Homework #3: Submission Deadline 9th March (10:00 PM)


1. Determine the Thevenin and Norton equivalent circuits of the following network between nodes a and b , and then determine the available power of the network.



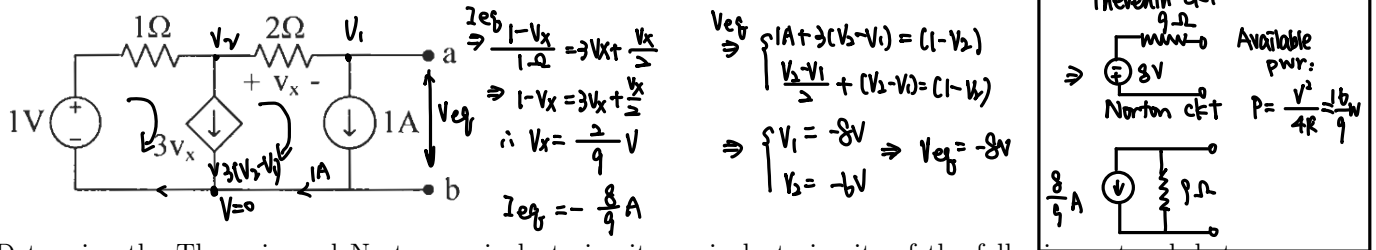
2. Determine the Thevenin and Norton equivalent circuits of the following network between nodes a and b , and then determine the available power of the network.



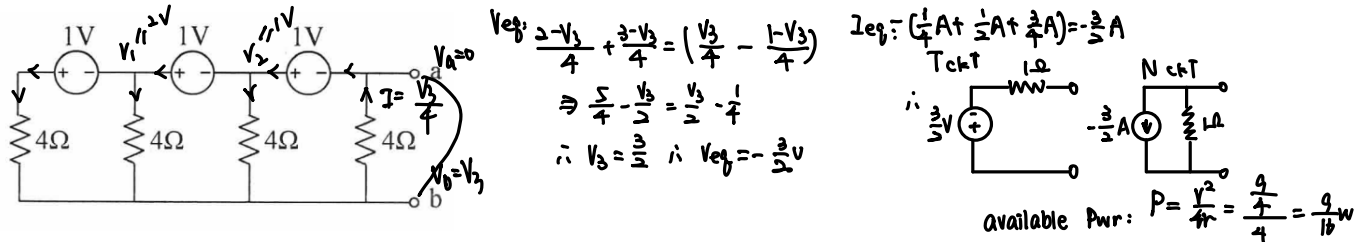3. Determine the Thevenin and Norton equivalent circuits of the following network between nodes a and b , and then determine the available power of the network.




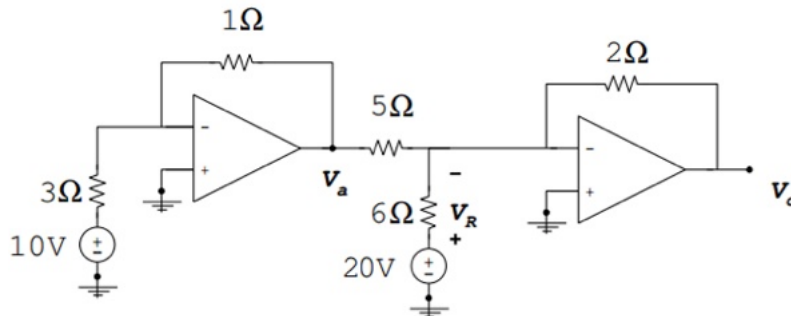4. In the op-amp circuit shown below, determine the voltages V_a , V_R , and V_o . Assume the circuit behaves linearly and make use of the ideal op-amp approximation.



- ① For V_a approximation:
- $$\frac{10V - V_a}{3\Omega} = \frac{V_a - V_R}{1\Omega} \Rightarrow V_a = -\frac{10}{3} V$$
- ② for V_R approximation:
- $$\frac{V_a}{5} + \frac{20}{6} = \frac{-V_o}{2} \Rightarrow V_o = -\frac{16}{3} V$$

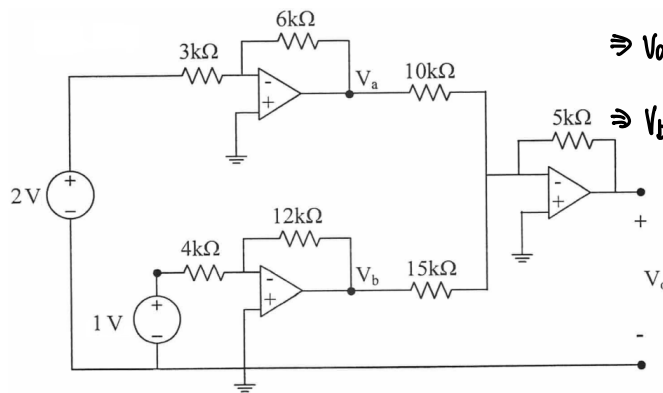5. In the op-amp circuit shown below, determine the voltages V_a , V_b , and V_o , assuming linear operation and the ideal op-amp approximation.




$$\Rightarrow V_a = -\frac{2V}{3k\Omega} \times 6k\Omega = -4V$$

$$\Rightarrow V_b = -\frac{1V}{4k\Omega} \times 12k\Omega = -3V$$

$$\Rightarrow \frac{-4V}{10k\Omega} + \frac{-3V}{15k\Omega} = \frac{-V_o}{5k\Omega}$$

$$\therefore V_o = 4 \times \frac{1}{2} + 3 \times \frac{1}{3} = 3V$$

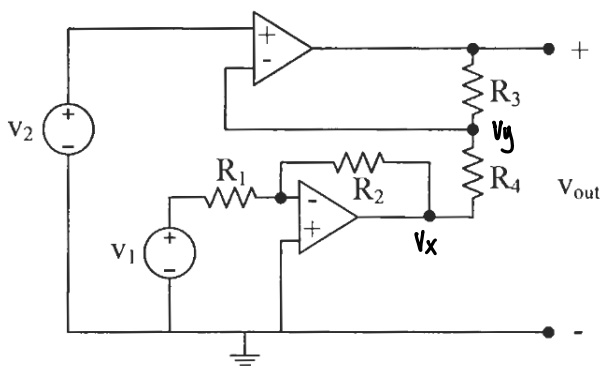6. Consider the circuit below assuming linear operation and the ideal op-amp approximation. Obtain v_{out} in terms of v_1 , v_2 , R_1 , R_2 , R_3 , and R_4 .



$$\Rightarrow V_x = -\frac{R_2}{R_1} V_1 \quad V_- \approx V_+ = V_2$$

$$\frac{V_2 - V_{out}}{R_3} = \frac{V_x - V_2}{R_4} \Rightarrow V_2 \left(\frac{R_3 R_4}{R_3 + R_4} \right) - V_x / R_4 = \frac{V_{out}}{R_3}$$

$$\therefore V_{out} = \left(1 + \frac{R_2}{R_1} \right) V_2 + \frac{R_3}{R_4} \cdot \frac{R_2}{R_1} V_1$$