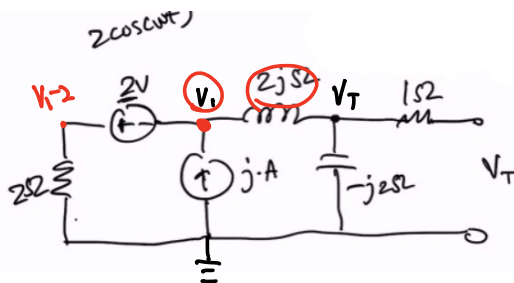


for impedance Network.

Node voltage and loop current
method to find open-circuit voltage
and short-circuit current



Apply KCL to the V_1 node

$$\frac{V_1 + 2}{2} + \frac{V_1 - V_T}{2j} = j$$

Apply KCL to V_T node


$$\frac{V_T}{1} + \frac{V_T - V_1}{2j} = 0$$

$V_1 = 0$ shorted

$$1 + \frac{V_T}{2j} = 1j$$

$$\Rightarrow 1 - j = \frac{V_T}{2j}$$

$$V_T = 2j(1 - j) = 2 + 2jV$$

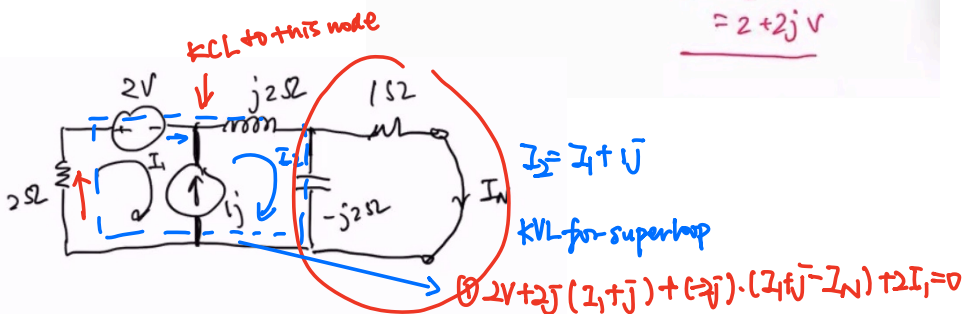


$$-2 + 2j(I_1 + j) - 2j(I_1 + j - I_N) + 2I_1 = 0$$

$$2I_N(1 - 2j) = 2(1 - jI_1)$$

$$I_N = \frac{1 + jI_1}{1 - 2j} A$$

$$Z_T = \frac{V_T}{I_N} = 3 - 2j \Omega \quad V_T = 2 + 2j$$

Thevenin equivalent

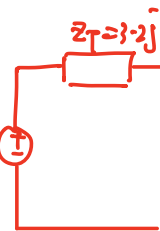

Average power

$$p = v \cdot i$$


$$p(t) = v(t) \cdot i(t)$$

Instantaneous power at a particular time

ω -sinusoidal \rightarrow steady-state
power absorbed by acbt element
by - average.

$$P = \frac{1}{T} \int_0^T v(t) \cdot i(t) dt$$

$$= \frac{1}{T} \int_0^T v(t) i(t) dt = \frac{1}{T} \int_0^T |v| \cos(\omega t + \theta) \times |i| \cos(\omega t + \phi) dt$$

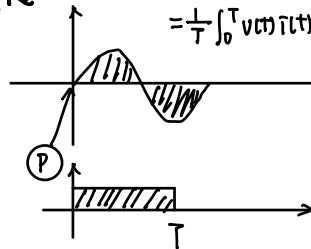

$$p(t) = v(t) \cdot i(t) = \text{Re}\{v e^{j\omega t}\} \cdot \text{Re}\{i e^{j\omega t}\} = \frac{v e^{j\omega t} + v^* e^{-j\omega t}}{2} \cdot \frac{i e^{j\omega t} + i^* e^{-j\omega t}}{2}$$

$$\begin{aligned} (C \cdot D)^* &= C^* \cdot D^* \\ (v i^*)^* &= v^* i \\ C &= v e^{j\omega t} \\ D &= i e^{-j\omega t} \end{aligned}$$

$$= \frac{v_1 e^{j\omega t} + v_1^* e^{-j\omega t}}{2} \cdot \frac{i_1 e^{j\omega t} + i_1^* e^{-j\omega t}}{2} = \frac{v_1 i_1 e^{j2\omega t} + v_1^* i_1^* e^{-j2\omega t} + v_1 i_1^* + v_1^* i_1}{4}$$

$$= \frac{v_1 i_1^* + v_1^* i_1}{4} = \frac{1}{4} \text{Re}\{v i^*\} + \frac{1}{4} \text{Re}\{v^* i\}$$

$$p(t) = \frac{1}{4} \text{Re}\{v i^*\} + \frac{1}{4} \text{Re}\{v^* i\}$$

$T = \frac{1}{2} T \quad \omega = 2\omega$

Part 2

$$p(t) = v(t) \cdot i(t) = \frac{1}{2} \text{Re}\{v \cdot i^*\} + \frac{1}{2} \text{Re}\{v^* \cdot i\}$$



average power over time:

$$P = \frac{1}{T} \int_0^T p(t) dt = \frac{1}{T} \int_0^T \frac{1}{2} \text{Re}\{v \cdot i^*\} dt + \frac{1}{T} \int_0^T \frac{1}{2} \text{Re}\{v^* \cdot i\} dt$$

$\Rightarrow \frac{1}{2} \text{Re}\{v \cdot i^*\}$ (const.)
 $\Rightarrow P = \frac{1}{2} \text{Re}\{v \cdot i^*\}$
Average power.

$|v| \cdot |i| \cos(2\omega t + \theta + \phi)$

Available Power

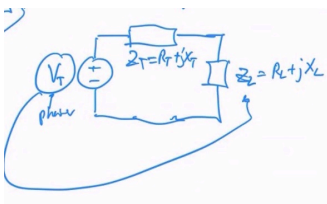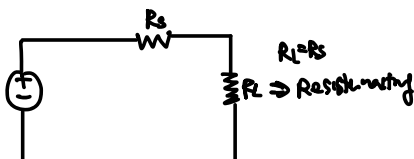

$$v_L = Z_L \cdot i_L$$

$$= \frac{V_T}{Z_T + Z_L} \cdot Z_L$$

$$C \cdot C^* = |C|^2$$

$$Z_L = R_L + jX_L$$

$$P = \frac{1}{2} \text{Re}\{v_L \cdot i_L^*\}$$

$$= \frac{1}{2} \text{Re}\left\{ \frac{V_T Z_L}{Z_T + Z_L} \cdot \frac{V_T^*}{(Z_T + Z_L)^*} \right\} = \frac{1}{2} \text{Re}\left\{ \frac{|V_T|^2 Z_L}{|Z_T + Z_L|^2} \right\} = \frac{1}{2} \text{Re}\left\{ \frac{|V_T|^2 R_L + j |V_T|^2 X_L}{|Z_T + Z_L|^2} \right\}$$

$$|a+jb|^2 = a^2+b^2$$

$$P = \frac{1}{2} \frac{|V_T|^2 R_L}{|(R_T + jX_T + j(-X_L))|^2}$$

$$\frac{V}{0} \Rightarrow X_T = -X_L$$


$$\Rightarrow P = \frac{1}{2} \frac{|V_T|^2 R_L}{(R_T + R_L)^2} \Rightarrow R_T = R_L$$

$$\Rightarrow P_{max} = \frac{|V_T|^2 R_L}{4R_L^2} = \frac{V_T^2}{4R}$$

$$P = \frac{1}{2} \frac{|V_T|^2 R_L}{|Z_L + Z_T|^2}$$

$$P = \frac{1}{2} \frac{|V_T|^2 R_L}{|Z_L + Z_T|^2}$$

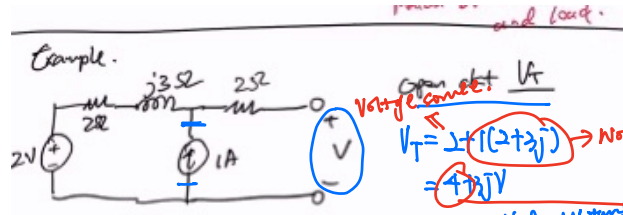Find the condition under which power of the load is maximized.



Voltage across V_T

$$V_T = 2 + 1(2 + j3) \rightarrow \text{Norton}$$

$$= 4 + j3V$$

Superposition by turning on sources one at a time.

$$Z_T = 2 + 2 + j3 = 4 + j3$$

$$\Rightarrow Z_L = 4 - j3 \quad P_{max} = \frac{|V_T|^2}{8R_T} = \frac{4^2 + 3^2}{8 \cdot 4}$$

$$= \frac{25}{32} W$$

$$\begin{cases} R_T = R_L \\ X_T = -X_L \Rightarrow Z_T = Z_L^* \end{cases}$$