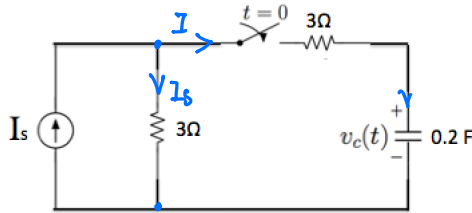


ECE-210 Analog Signal Processing Spring 2022

Homework #4: Submission Deadline 16 th March (10:00 PM)

1. In the next circuit,  $v(t) = 4\text{ V}$  for  $t < 0$ . Determine  $v(t)$  for  $t > 0$  after the switch is closed, and identify the zero-state and zero-input components of  $v(t)$ . (Hint:  $I_s$  donates a DC current source)



$$Q = CU \Rightarrow \frac{dQ}{dt} = \bar{i}$$

$$(I_s - C \frac{dv_c(t)}{dt}) \cdot 3\Omega = C \frac{dv_c(t)}{dt} \cdot 3\Omega + V_c(t)$$

$$\Rightarrow 6C \frac{dv_c(t)}{dt} + V_c(t) = 3I_s$$

$$\Rightarrow \frac{dV_c(t)}{dt} + \frac{1}{6C} V_c(t) = 3I_s$$

Zero Input  $\Leftrightarrow I_s = 0$


$$\Rightarrow V_c(t) = A e^{-\frac{1}{6C}t}$$

$$= A e^{-\frac{5}{6}t}$$

$$A = V_c(0) \Rightarrow V_c(t) = 4 e^{-\frac{5}{6}t} \text{ V}$$

2. The circuit shown below is in DC steady-state before the switch flips at  $t = 0$

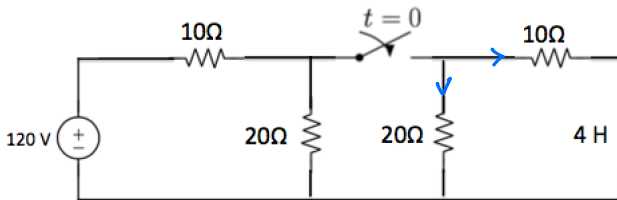- (a) Find  $V_L(0^-)$ ,  $V_L(t \rightarrow \infty)$ ,  $i_L(0)$ , and  $i_L(t \rightarrow \infty)$   
 (b) Find  $i_L(t)$  and  $V_L(t)$ .  
 (c) Sketch  $i_L(t)$  and  $V_L(t)$ . Identify discontinuities.



(a)  $V_L(0^-) = 60\text{ V}$     (b)  $\frac{dV_L}{dt} + 10\Omega \cdot i_L = 5(12 - i_L)$   
 $V_L(t \rightarrow \infty) = 0\text{ V}$      $\Leftrightarrow \frac{di_L}{dt} + 15\Omega \cdot i_L = 60 \Rightarrow \frac{di_L}{dt} + \frac{15}{4} i_L = 15$   
 $i_L(0) = 0\text{ A}$      $i_L(t \rightarrow \infty) = 4\text{ A}$

$$\Rightarrow i_L(t) = [15 \int \frac{1}{15} e^{-\frac{15}{4}t} dt + C] \cdot e^{-\frac{15}{4}t}$$

$$= [15 \cdot \frac{4}{15} (1 - e^{-\frac{15}{4}t}) + C] e^{-\frac{15}{4}t}$$


$$= [4 + C e^{-\frac{15}{4}t}] e^{-\frac{15}{4}t}$$

$$= 4 + C e^{-\frac{15}{4}t}$$

$V_L(t) = L \frac{di_L}{dt} = 4 \frac{di_L}{dt}$

$$= 4 \cdot \frac{15}{4} e^{-\frac{15}{4}t} = 15 e^{-\frac{15}{4}t}$$

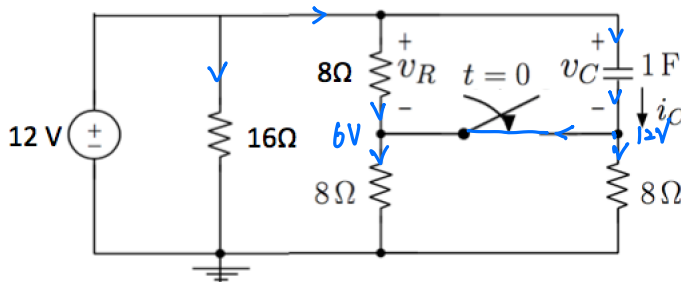3. The circuit shown below has been in DC steady-state before the switch closes at  $t=0$ . Find  $V_c(t)$  and  $i_c(t)$ .



$$C \frac{dV_c}{dt} + \frac{V_c}{8\Omega} = \frac{12 - V_c}{8\Omega} + \frac{12 - V_c}{8\Omega}$$

$$C \frac{dV_c}{dt} + \frac{3V_c}{8} = 3$$


$$\frac{dV_c}{dt} + \frac{3V_c}{8} = 3$$

$$V_c = V_R$$

$$\Rightarrow V_c = V_R = \int 3 e^{-\frac{3}{8}t} dt + C = 8 e^{-\frac{3}{8}t} + C$$

$$= 8 + C e^{-\frac{3}{8}t}$$

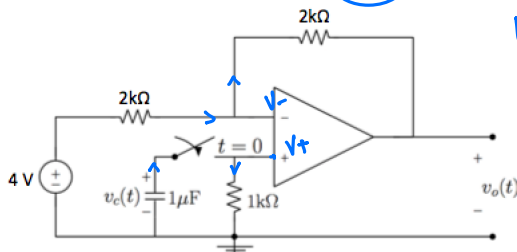4. Assume linear operation and  $V_c(0) = -1\text{ V}$ , determine  $V_o(t)$  in the following circuit:



$V_o(t)|_{t=0} = -4\text{ V}$

$$\frac{4 - V_o}{2k\Omega} = \frac{V_o - V_o}{2k\Omega}$$

$$V_o \approx V_o \approx 0$$

$$\Rightarrow V_o = -4\text{ V}$$

$$\Rightarrow \frac{4 - V_o(t)}{2k\Omega} = \frac{V_o(t) - V_o(t)}{2k\Omega} \Rightarrow V_o(t) = 2V_c(t) - 4$$

$$-C \frac{dV_c(t)}{dt} = \frac{V_c(t)}{R} \Rightarrow \frac{dV_c(t)}{dt} + \frac{1}{RC} V_c(t) = 0$$

$$\Rightarrow V_c(t) = A e^{-\frac{1}{RC}t}$$

$$V_c(0) = A = -1\text{ V}$$

$$\Rightarrow V_c = -e^{-\frac{1}{RC}t}$$

$$\Rightarrow V_o(t) = -2e^{-\frac{1}{RC}t} - 4\text{ V}$$

$$= -2e^{-1000t} - 4\text{ (V)}$$